

Electrostatics and Circuits:

<u>Variable</u>	<u>Unit</u>
P	$W = \frac{J}{s}$
E	J
$q \text{ or } Q$	C
R	Ω
\vec{E}	N/C
V	V =
I	$A = \frac{C}{s}$
F	N
constant: k	$N \cdot m^2 / C^2$
r	m
d	m
ΔU_e	J

Find all V's and I's:



$R_1 = 70 \Omega$

$R_2 = 90 \Omega$

$R_3 = 110 \Omega$


$R_4 = 85 \Omega$

$R_5 = 92 \Omega$

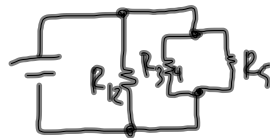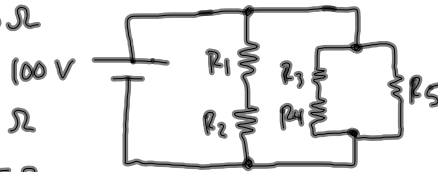

$R_{12} = 160 \Omega$

$R_{34} = 175 \Omega$

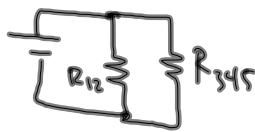


$R_{345} = 62.5 \Omega$



$R_{eq} = 44.9 \Omega$
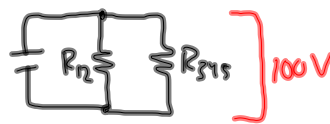
$$V_{total} = I_{total} R_{eq} \quad I_{total} = \frac{100V}{44.9 \Omega} = 2.23 A$$



$I_{12} = \frac{100V}{R_{12}} = 0.625 A$

$I_{345} = \frac{100V}{R_{345}} = 1.6 A$




$V_1 = I_{12} R_1 = 43.8 V$

$V_2 = I_{12} R_2 = 56.2 V$

$I_5 = \frac{100V}{R_5} = 1.09 A$

equivalent circuits

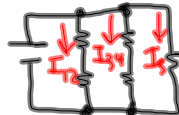

$I_{total} = I_{12} + I_{34} + I_5$

$I_{34} = 2.2 A - 0.625 A - 1.09 A$


$= 0.51 A$

$$V_3 = I_{34} R_3$$


$$= 56.1 V$$

$$V_4 = I_{34} R_4$$

$$= 43.9 V$$

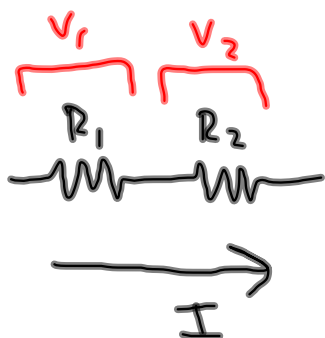

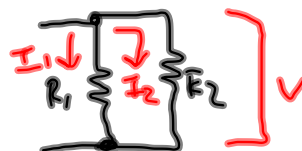Series connections:
share current
different V 's




parallel connections:
share voltage
different I 's

Electrostatics and Circuits Review 1st Block 11.17.11

Three charges are arranged in a line. Charge 1 has a value of -90 microC and is located at the origin, charge 2 has a value of +80 microC and is located at $x = 2$ cm, and charge 3 has a value of -60 microC and is located at $x = 5$ cm.

a) Find the value of the electric field at the point $x = 10$ cm.

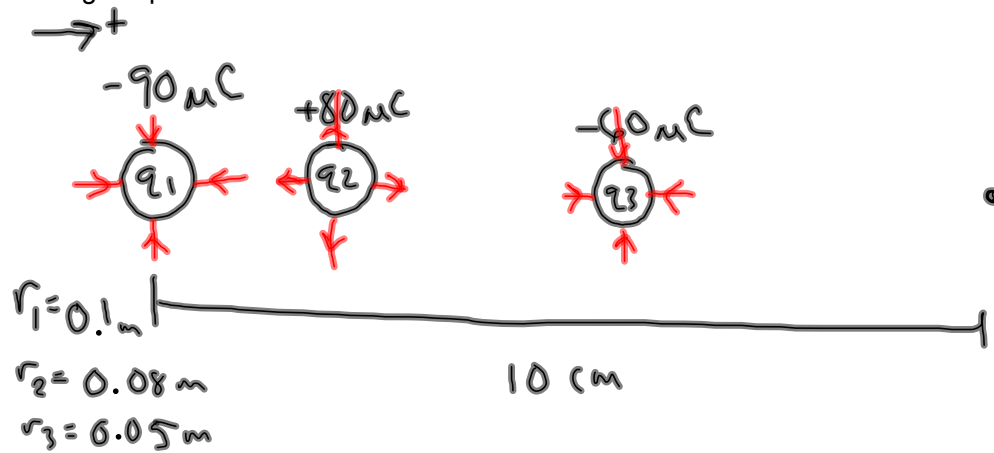b) If a charge of +50 microC is placed at this point, what is the electric force that the charge experiences?



$$a) \bar{E}_{\text{net}} = \bar{E}_1 + \bar{E}_2 + \bar{E}_3$$

$$= -\frac{k|q_1|}{r_1^2} + \frac{k|q_2|}{r_2^2} + \frac{-k|q_3|}{r_3^2}$$


$$= (8.77 \times 10^9 \text{ N}\cdot\text{m}^2/\text{C}^2) \left[-\frac{(90 \times 10^{-6} \text{ C})}{(0.1 \text{ m})^2} + \frac{(80 \times 10^{-6} \text{ C})}{(0.08 \text{ m})^2} - \frac{(60 \times 10^{-6} \text{ C})}{(0.05 \text{ m})^2} \right]$$

$$= -1.84 \times 10^8 \text{ N/C}$$

$$b) \bar{E} = \frac{\bar{F}}{q}$$

$$\bar{F} = \bar{E} q = (-1.84 \times 10^8 \text{ N/C})(+50 \times 10^{-6} \text{ C})$$

$$= -9215 \text{ N}$$

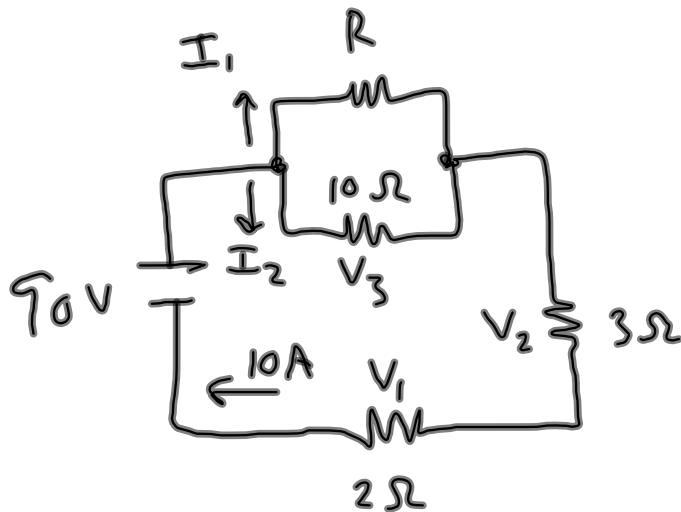

$$\begin{aligned}
 R &= \\
 V_3 &= 40\text{ V} \\
 V_2 &= 30\text{ V} \\
 V_1 &= 20\text{ V} \\
 I_1 &= 6\text{ A} \\
 I_2 &= 4\text{ A}
 \end{aligned}$$

$$I_{\text{total}} = 10\text{ A}$$

$$10\text{ A} = I_1 + I_2$$

$$V_1 = I_{\text{total}}(2\Omega) = 20\text{ V}$$

$$I_1 = 6\text{ A}$$

$$V_2 = I_{\text{total}}(3\Omega) = 30\text{ V}$$

$$\begin{aligned}
 V_{\text{total}} &= V_1 + V_2 + V_3 \Rightarrow V_3 = 90\text{ V} - 20\text{ V} - 30\text{ V} \\
 &= 40\text{ V}
 \end{aligned}$$

$$I_2 = \frac{V_3}{10\Omega} = 4\text{ A}$$